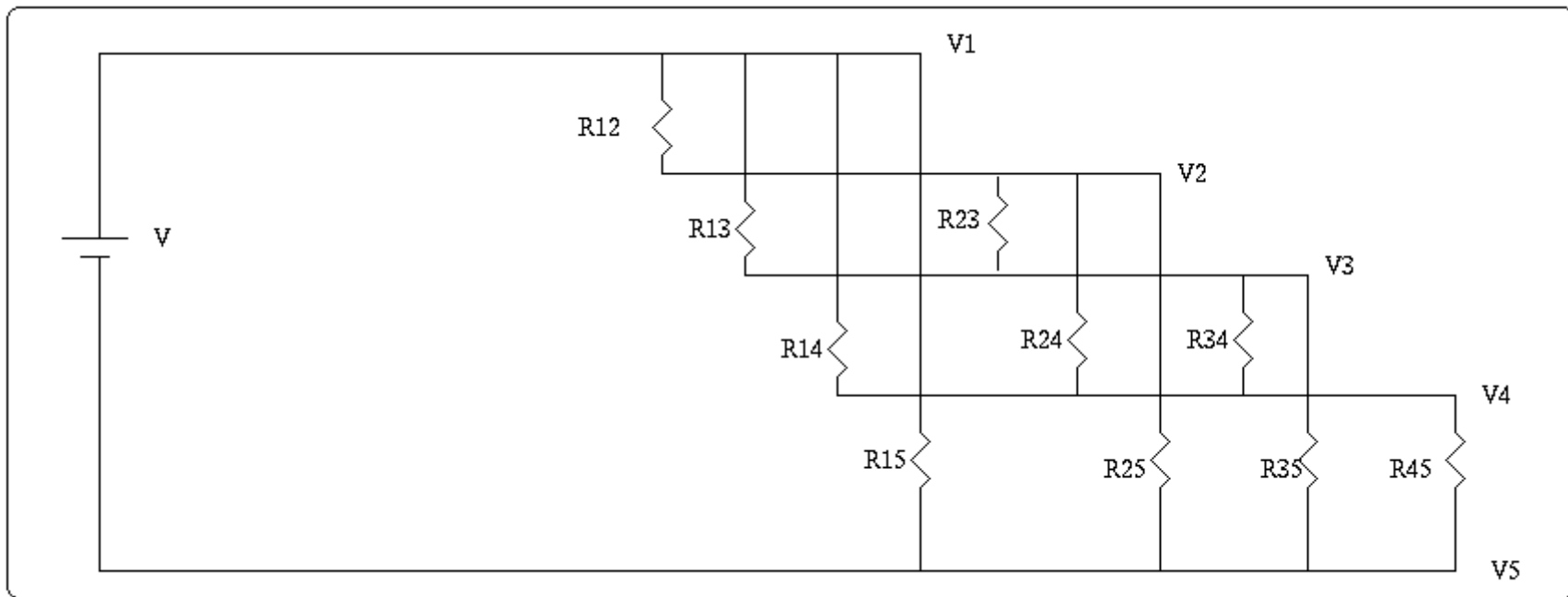


Phys699 - Statistical Methods in Data Analysis - Assignment #I



Given the above circuit it is possible to calculate the total current (I) applying Krichoff's laws

$$I = \sum_{i=1}^5 (V_1 - V_i) \frac{1}{R_{1i}}$$

$$0 = \sum_{i=1}^5 (V_2 - V_i) \frac{1}{R_{2i}}$$

$$0 = \sum_{i=1}^5 (V_3 - V_i) \frac{1}{R_{3i}}$$

$$0 = \sum_{i=1}^5 (V_4 - V_i) \frac{1}{R_{4i}}$$

where $\frac{1}{R_{ii}} = 0$

To solve for the 4 unknowns (I, V_2, V_3 and V_4) the last 3 equations may be re-arranged...

Phys699 - Statistical Methods in Data Analysis - Assignment #1

$$-\sum_{i=1}^5 \frac{1}{R_{2i}} V_2 + \frac{1}{R_{23}} V_3 + \frac{1}{R_{24}} V_4 = -\frac{1}{R_{12}} V$$

$$\frac{1}{R_{23}} V_2 - \sum_{i=1}^5 \frac{1}{R_{3i}} V_3 + \frac{1}{R_{34}} V_4 = -\frac{1}{R_{13}} V$$

$$\frac{1}{R_{24}} V_2 + \frac{1}{R_{34}} V_3 - \sum_{i=1}^5 \frac{1}{R_{4i}} V_4 = -\frac{1}{R_{14}} V$$

where the identities $V_1 = V$ and $V_5=0$, have been applied.

Numerical methods can be used to find the voltages V_2, V_3 and V_4 and, when substituted into the first equation on the previous page, the total current I .

Produce a program that solves this problem for any number of voltage points between 3 and 20. Note the case when $V=1$ Volt, all resistors are present, and the value of the resistors are:

$$R_{ij} = |i - j| \Omega$$

Provide the following in your solution:

- a description of the problem
- development of your algorithm
- all code (use standard, concise and efficient coding practices).
- a final plot of current vs. number of voltage points

Hint: consider algorithms that apply matrix decomposition.